

ELE 215

Linear Circuits Laboratory




Recitation 9
Circuit Discovery
Useful for BB

Terminology, Circuit Analysis

- Consider the RC circuit
- From phasor analysis

$$H(\omega) = \frac{1/j\omega C}{R + 1/j\omega C}$$
$$= \frac{1}{1 + j\omega RC}$$




Lowpass filter

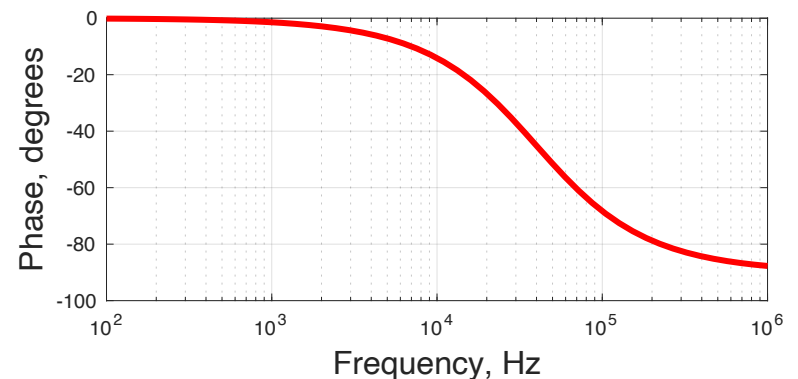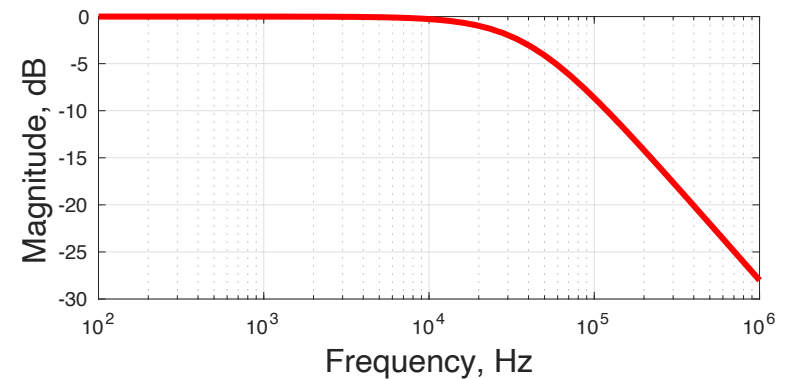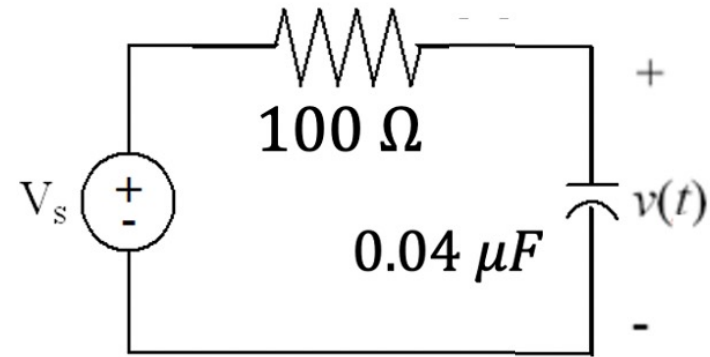

Now, Circuit Discovery

- But what if C is not known?
- Can we find it from some measurements?
- Take some data (limited accuracy)

freq	amp	phase
100 Hz	1.00	0°
1 kHz	1.00	-1.5°
10 kHz	0.95	-14°
100 kHz	0.35	-68°
1 MHz	0.05	-88°

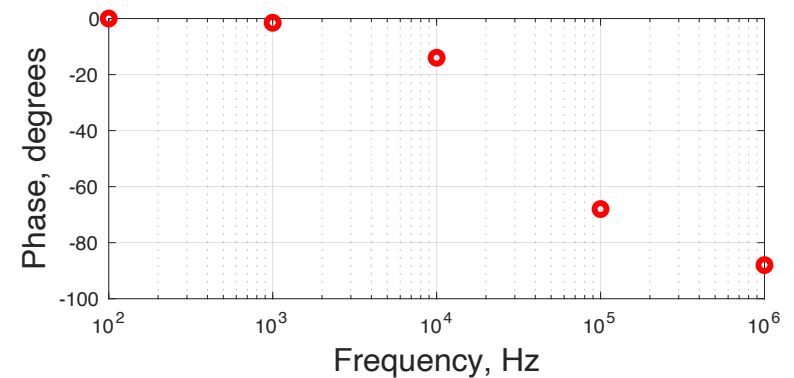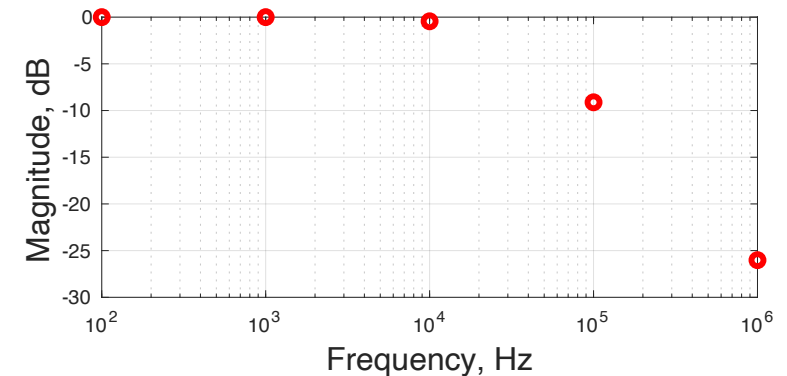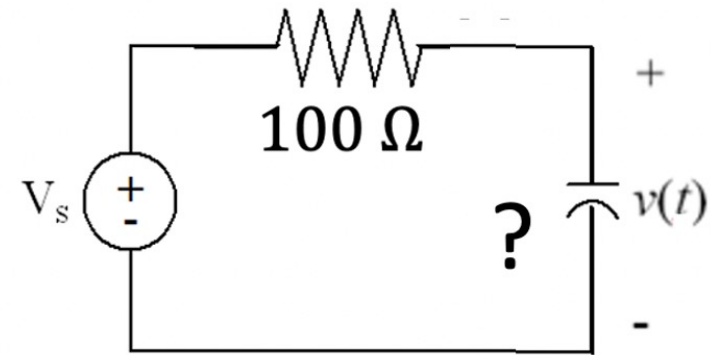

- If it's a simple circuit, then we could “do the math”:

– The k^{th} measurement pair is

$$A_k = \frac{1}{\sqrt{1 + (\omega_k RC)^2}} = \frac{1}{\sqrt{1 + (100 \omega C)^2}}$$

$$\text{or} \quad C = \frac{1}{100 \omega} \sqrt{\frac{1}{A^2} - 1}$$

$$\theta_k = -\tan^{-1}(\omega_k RC) = -\tan^{-1}(100 \omega C)$$

$$\text{or} \quad C = \frac{1}{100 \omega} \tan(-\theta)$$

$$C = \frac{1}{100 \omega} \sqrt{\frac{1}{A^2} - 1}$$


$$C = \frac{1}{100 \omega} \tan(-\theta)$$

freq	amp	C from amp
100 Hz	1.00	0
1 kHz	1.00	0
10 kHz	0.95	5.23×10^{-8}
100 kHz	0.35	4.26×10^{-8}
1 MHz	0.05	3.18×10^{-8}

freq	phase	C from phase
100 Hz	0°	0
1 kHz	-1.5°	4.17×10^{-8}
10 kHz	-14°	3.96×10^{-8}
100 kHz	-68°	3.94×10^{-8}
1 MHz	-88°	4.56×10^{-8}


Which value to use?

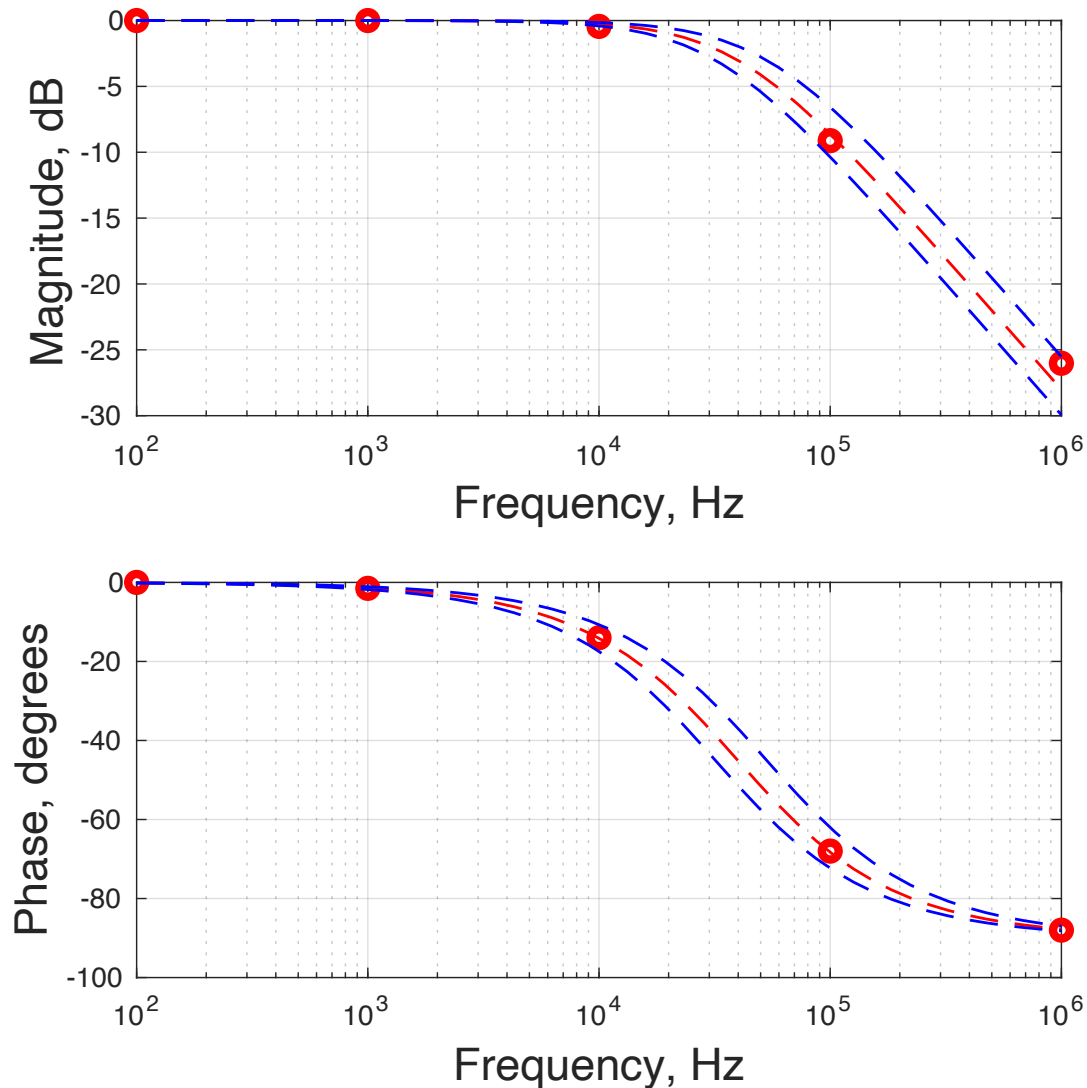- Or could “guess and check” graphically – try the values 30, 40, and 50 nF (red dots are data, dotted lines are guesses) – essentially, curve fitting



Application



- Lab 6 circuit:

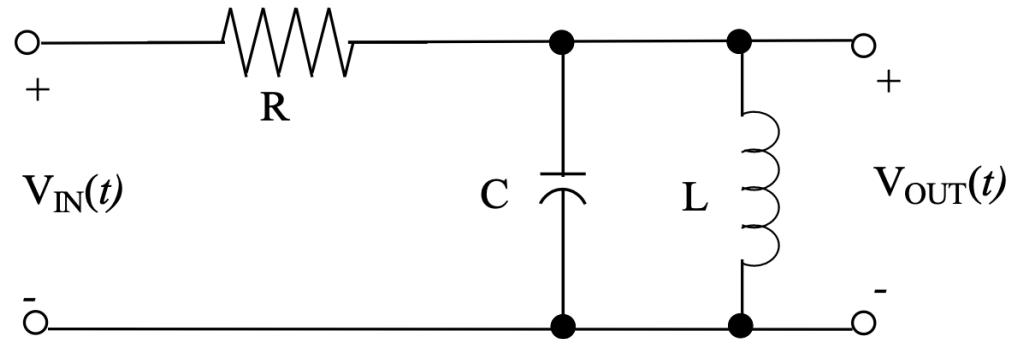


- My example:

- $R = 3909 \, \Omega$
- $L = 4.75 \, mH$
- $C = 9.46 \, nF$

- Looks good,
but...

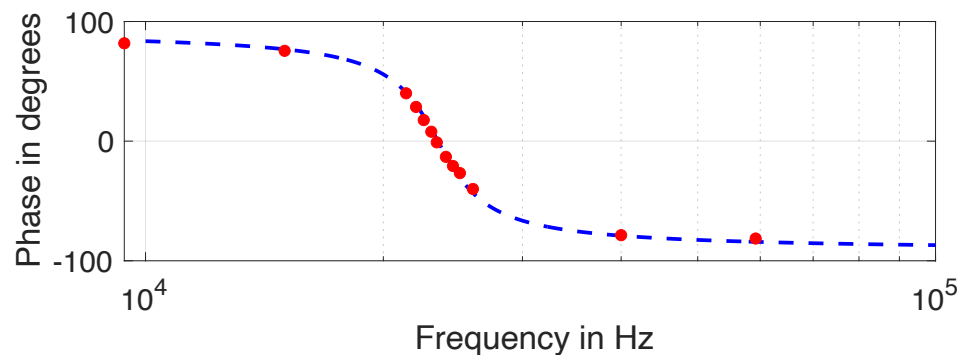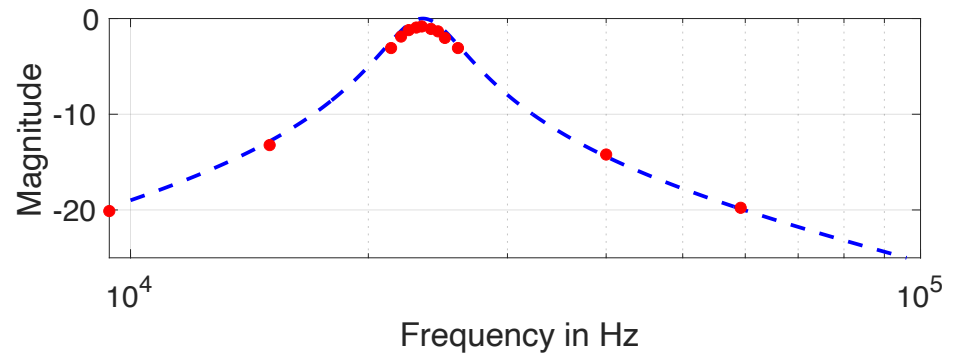


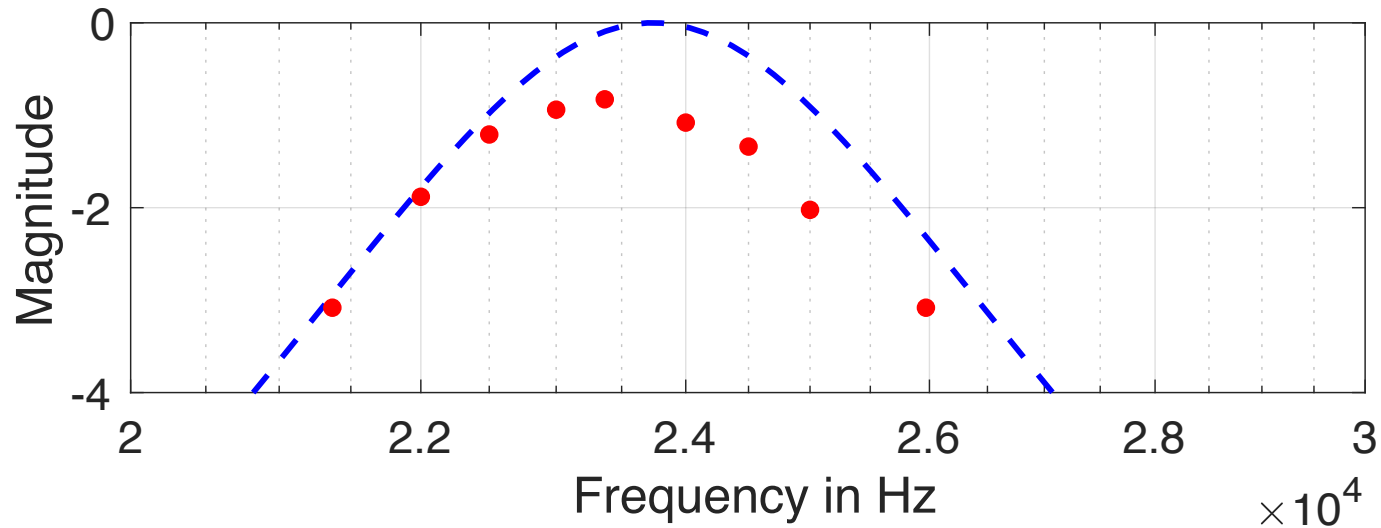- Upon closer inspection, the data is not a great fit near the peak



- Right general shape , but ...
 - Leftward shift ?
 - Downward shift ?


- What did we expect ?

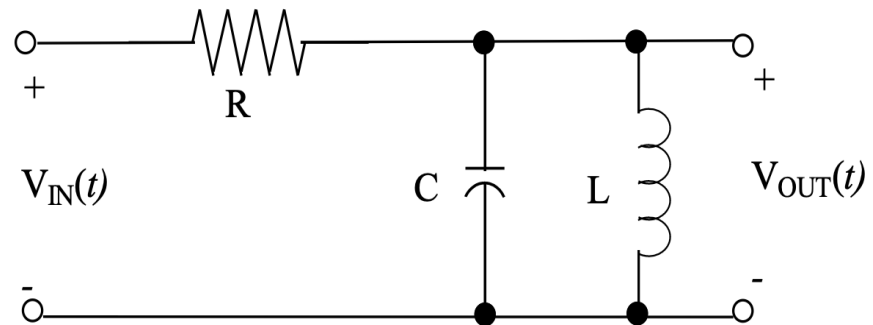


$$H(\omega) = \frac{Z_p}{R + Z_p} = \dots = \frac{1}{1 - j \frac{R(1 - \omega^2 LC)}{\omega L}}$$

- Peak of $|H(\omega)| = 1$ when $\omega^2 LC = 1$, so left/right shift is likely an error in the inductor value


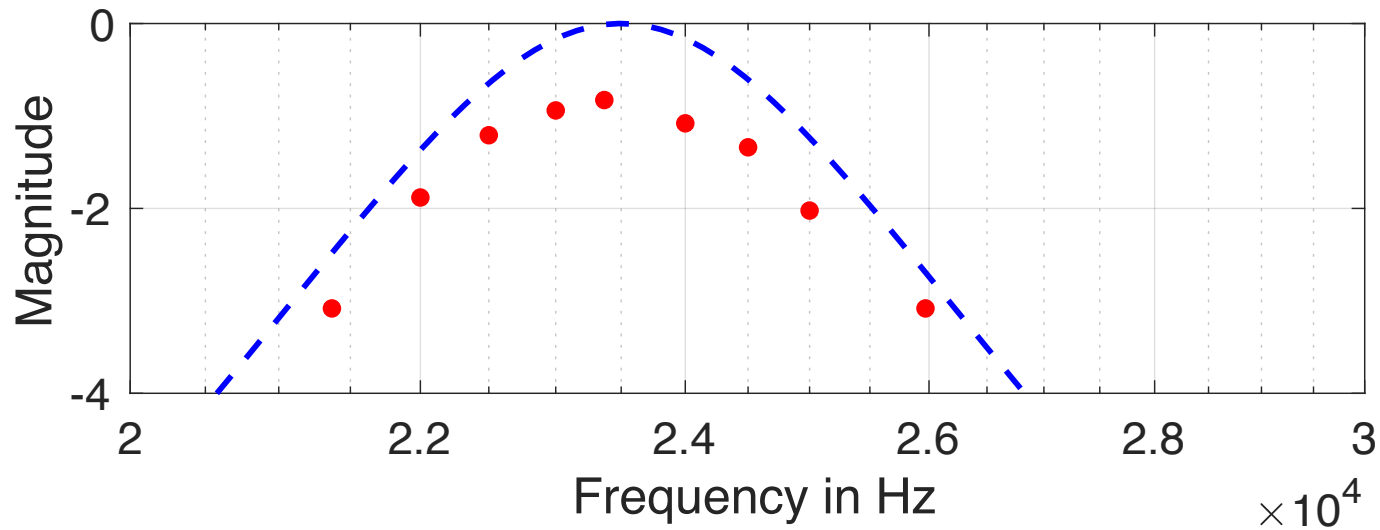
- Using 4.85 mH (found by “guess and check”):



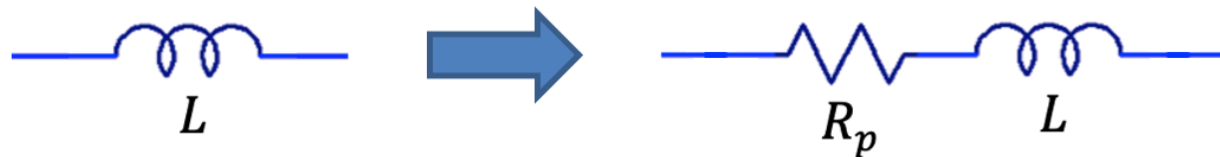- But what about the downward shift? Model the wire resistance in the inductor



- Including $R_p = 15\ \Omega$ (again, by guess and check)

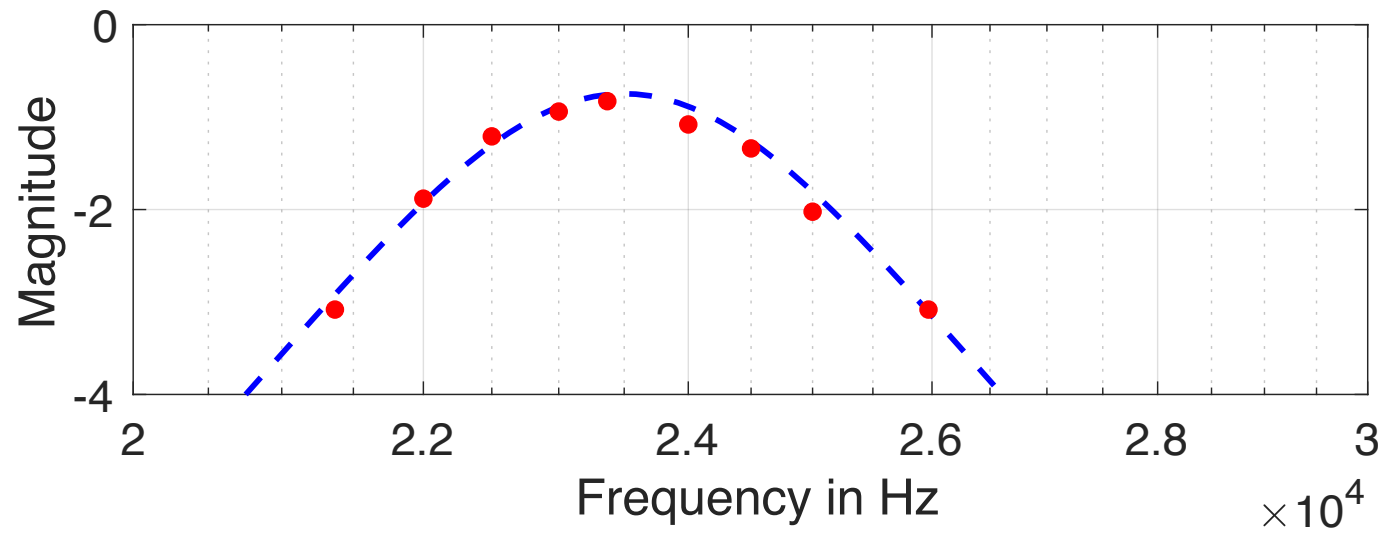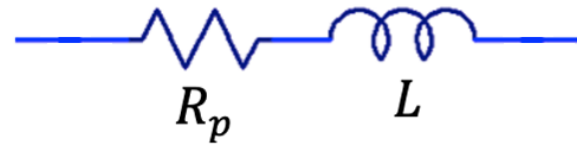


Lab 7 – A Notch Filter

- Type beyond LPF, BPF, HPF
- Typical use – to remove a specific signal from interfering with a system. E.g.:
 - 60 Hz from power grid
 - 88 kHz fish finder from a nav system

- Twin-T circuit:
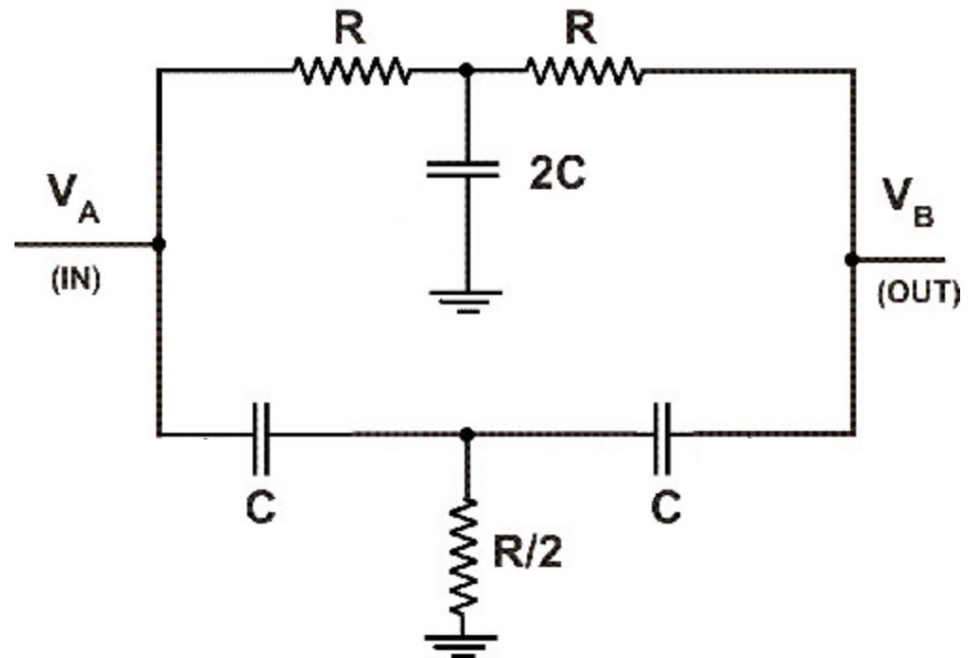
$$H(f) = \frac{V_B}{V_A} = \frac{1 - (2\pi fRC)^2}{(1 + j2\pi fRC)^2}$$



Specifics for next week

- Continue Exercise 1 – due April 6
- Prelab 7 for 9 AM Monday March 30 – 20 points
 - Theoretical characteristics of your BPF; expected Bode plot
 - Instructions posted on ELE 215 website
- Lab 7 – 80 points (pairs):
 - Instructions posted on ELE 215 website
 - Summary sheets available in lab rooms and on website
 - Due by 5 PM Wednesday April 8
- Exercise 4 – 50 points – same pairs as Lab 7
 - Getting a better fit to your Lab 7 data
 - See instructions/summary page on the ELE 215 website
 - Due by 5 PM Wednesday April 15