

ELE 215 Summary Report Form
Exercise 4 – due 5 PM on Apr 15, 2026

Score:


/ 50

Names: _____

HW IDs (just the last 3 digits): _____

1. Setup:

a) Components:

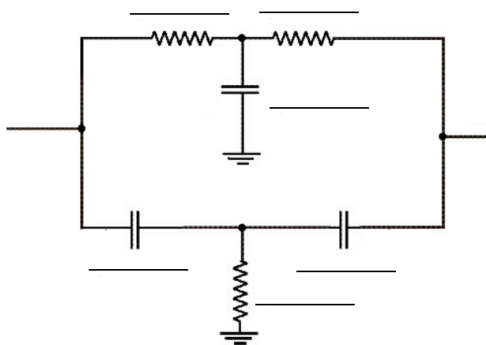

2. Your Lab 7 data:

frequency	Actual Frequency (Hz)	Gain (dB)	Phase Shift (degrees)
f_n			
-3 dB freq below f_n			
-3 dB freq above f_n			
-20 dB freq below f_n			
-20 dB freq above f_n			

Attach your Bode plot to this information page.