

ELE 215



Linear Circuits Laboratory

Recitation 6

scope measurements;
application to op amps

Scope Measurements

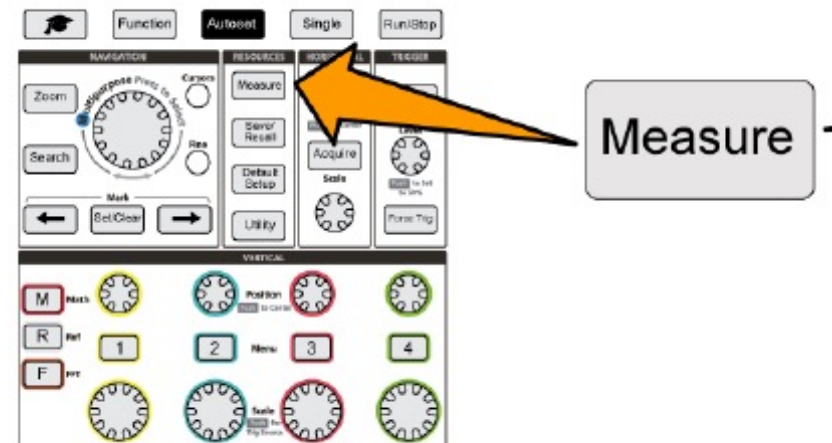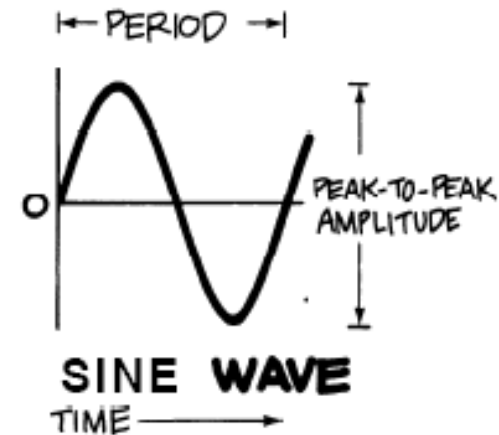- SigGen settings allow us to control the inputs to circuits
 - Frequency
 - Amplitude
 - Other
- How about measurement within the circuit?
 - Scope is the tool




- Common attributes of interest

- Time axis

- **Frequency**

- Period

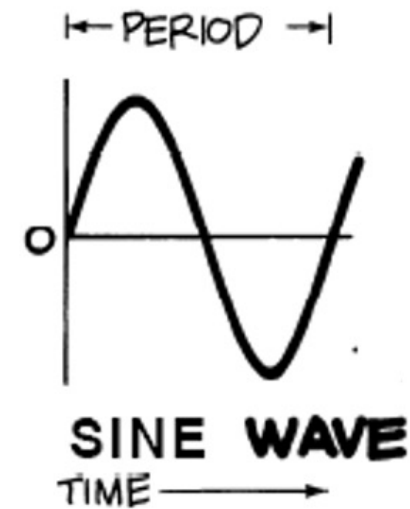


- Rise time

- Fall time


- Width

- Duty cycle

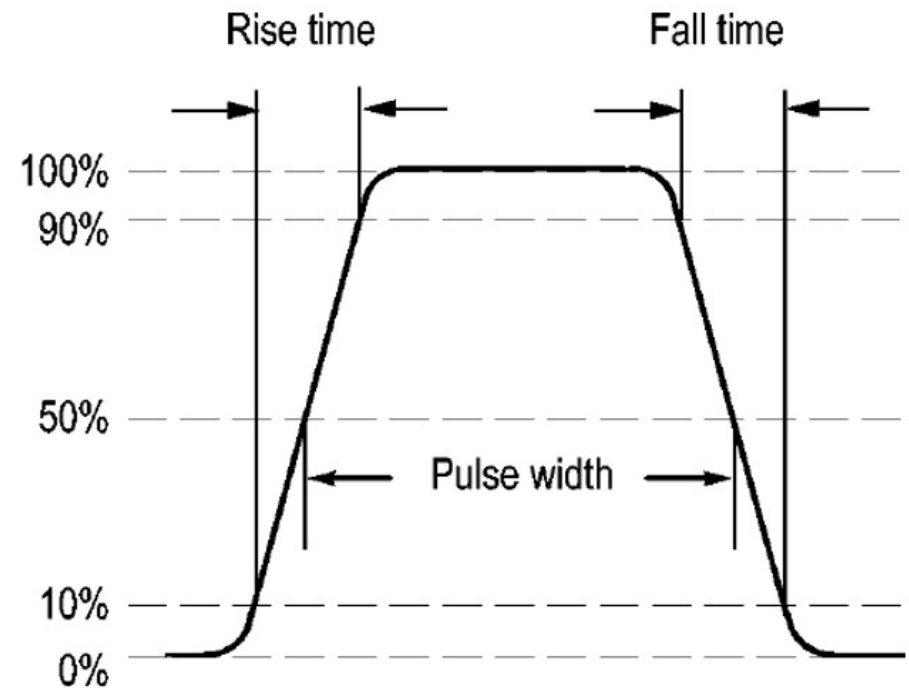


— Amplitude axis

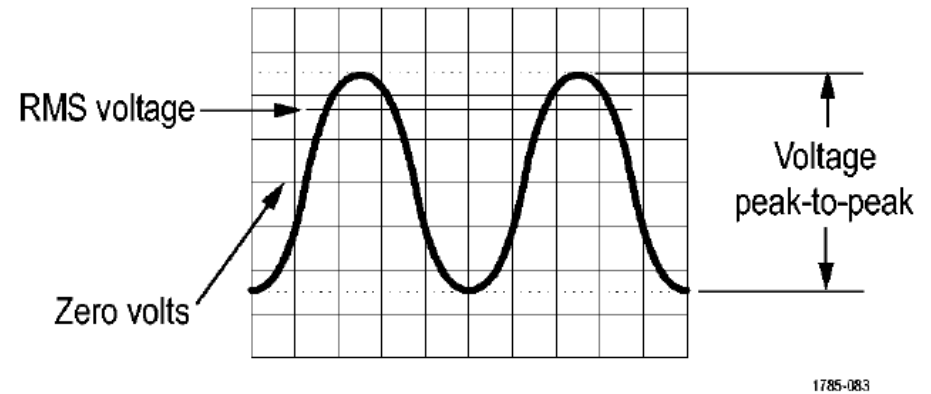- Peak-to-peak
- **Amplitude**
- Mean
- Max
- Min





— Between channels

- Delay
- **Phase**

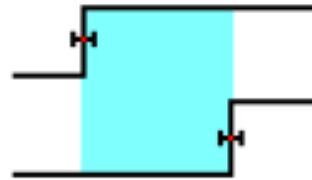


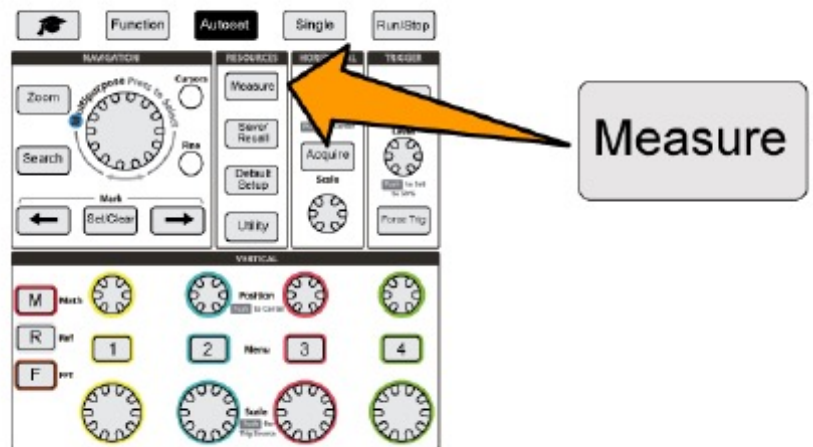
- How to choose?
- “Measure” button opens a window of choices
 - Use multipurpose knob to scroll to desired one; press multipurpose knob to select (or deselect)
 - Appears on the screen



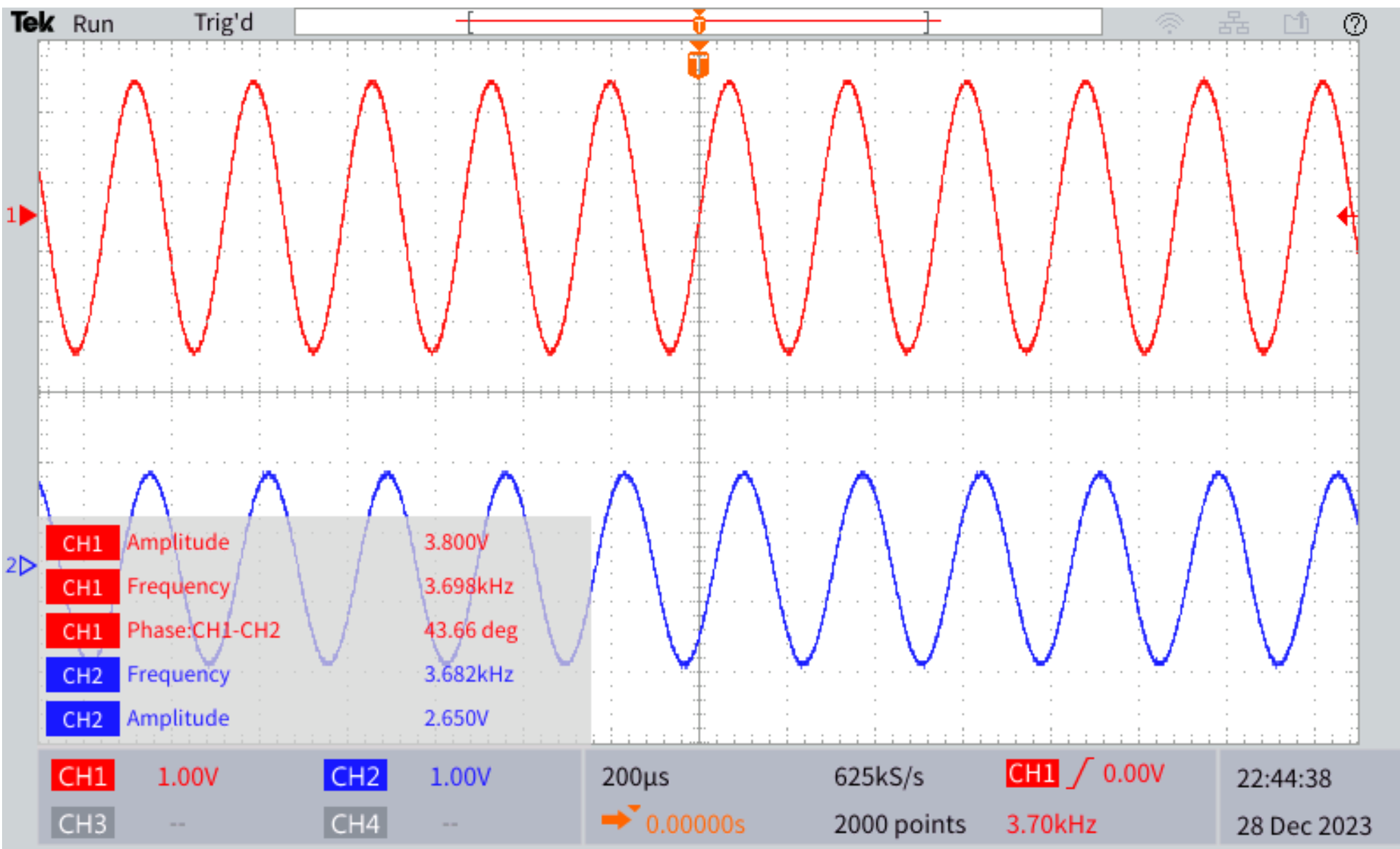


Op Amps

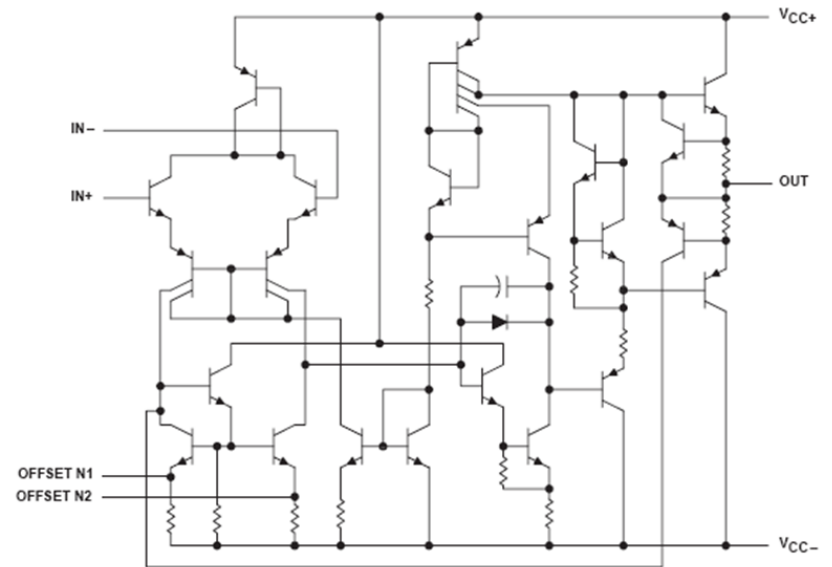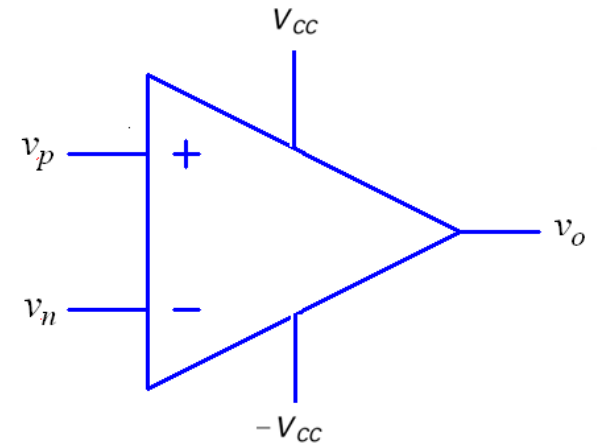
- A 3-terminal device (plus power connections)
- Introduced in the 1960's
- Commonly used to build amplifiers, math circuits, and filters
- Many versions exist:
 - 741
 - Low noise
 - ...



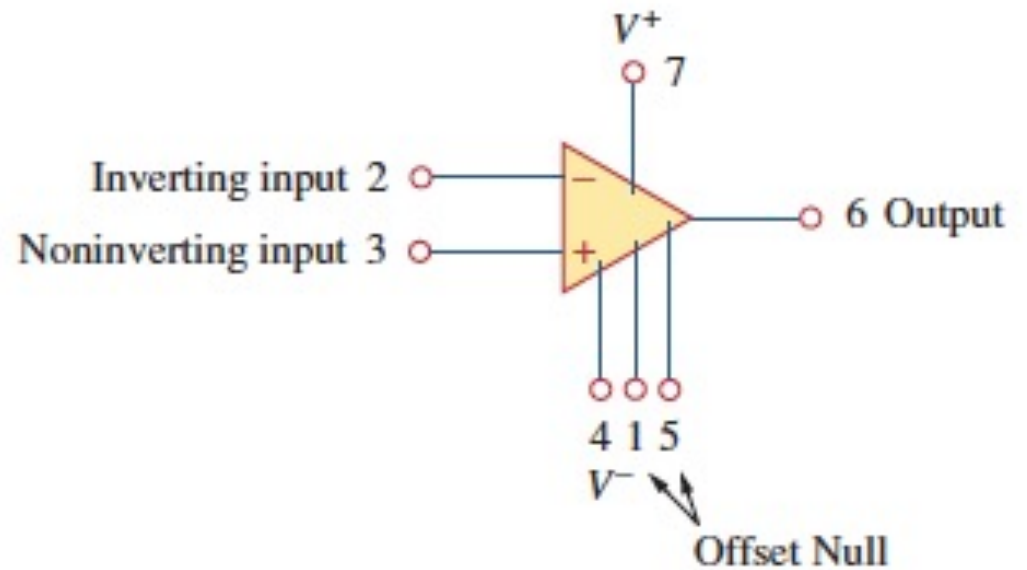- Connections:
 - + power ($+V_{cc}$)
 - – power ($-V_{cc}$)
 - Inverting input v_n
 - Non-inverting input v_p
 - Output v_o




circuit symbol.

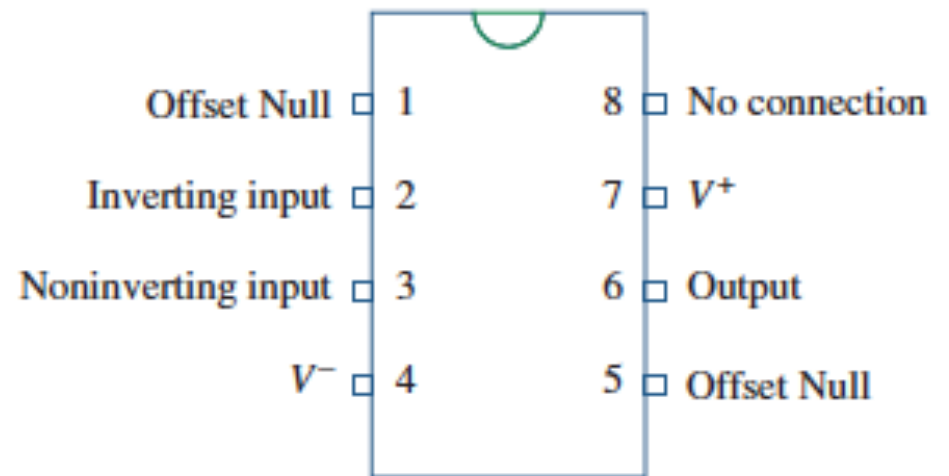

pin configuration.

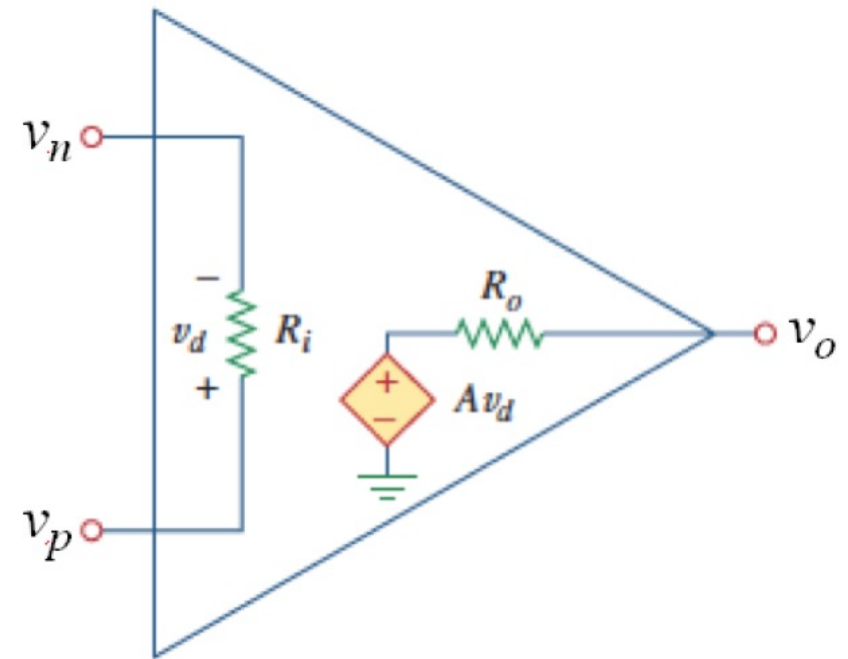- Nominally behaves like a voltage dependent voltage source



- Simplest circuit model:
 - Dependent voltage source
 - Control voltage is $v_d = v_p - v_n$
 - “Open loop” gain: A (is large, 10^5 or more)
 - Two resistors
 - “Input resistance” R_i : large ($10^5 \Omega$ or more)
 - “Output resistance” R_o : small (100Ω or less)

From the 741 Spec Sheet

electrical characteristics at specified free-air temperature, $V_{CC\pm} = \pm 15\text{ V}$, $T_A = 25^\circ\text{C}$ (unless otherwise noted)


| PARAMETER | | TEST CONDITIONS | $\mu\text{A}741\text{Y}$ | | | UNIT |
|-----------------------------|--|---|--------------------------|----------|----------|-----------------|
| | | | MIN | TYP | MAX | |
| V_{IO} | Input offset voltage | $V_O = 0$ | | 1 | 6 | mV |
| $\Delta V_{IO(\text{adj})}$ | Offset voltage adjust range | $V_O = 0$ | | ± 15 | | mV |
| I_{IO} | Input offset current | $V_O = 0$ | | 20 | 200 | nA |
| I_{IB} | Input bias current | $V_O = 0$ | | 80 | 500 | nA |
| V_{ICR} | Common-mode input voltage range | | ± 12 | ± 13 | | V |
| V_{OM} | Maximum peak output voltage swing | $R_L = 10\text{ k}\Omega$ | ± 12 | ± 14 | | V |
| | | $R_L = 2\text{ k}\Omega$ | ± 10 | ± 13 | | |
| A_{VD} | Large-signal differential voltage amplification | $R_L \geq 2\text{ k}\Omega$ | 20 | 200 | | V/mV |
| r_i | Input resistance | | 0.3 | 2 | | M Ω |
| r_o | Output resistance | $V_O = 0$, See Note 5 | | 75 | | Ω |
| C_i | Input capacitance | | | 1.4 | | pF |
| CMRR | Common-mode rejection ratio | $V_{IC} = V_{ICR\text{min}}$ | 70 | 90 | | dB |
| k_{SVS} | Supply voltage sensitivity ($\Delta V_{IO}/\Delta V_{CC}$) | $V_{CC} = \pm 9\text{ V to } \pm 15\text{ V}$ | | 30 | 150 | $\mu\text{V/V}$ |
| I_{OS} | Short-circuit output current | | | ± 25 | ± 40 | mA |
| I_{CC} | Supply current | $V_O = 0$, No load | | 1.7 | 2.8 | mA |
| P_D | Total power dissipation | $V_O = 0$, No load | | 50 | 85 | mW |

^T All characteristics are measured under open-loop conditions with zero common-mode voltage unless otherwise specified.


NOTE 5: This typical value applies only at frequencies above a few hundred hertz because of the effects of drift and thermal feedback.



- Experiences open loop “saturation”



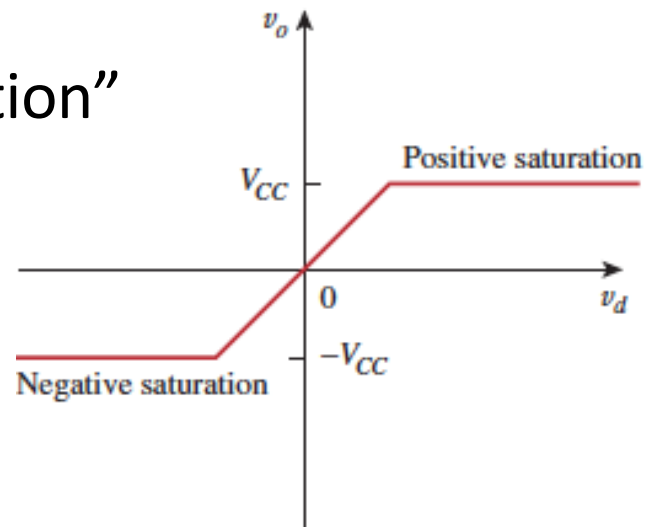


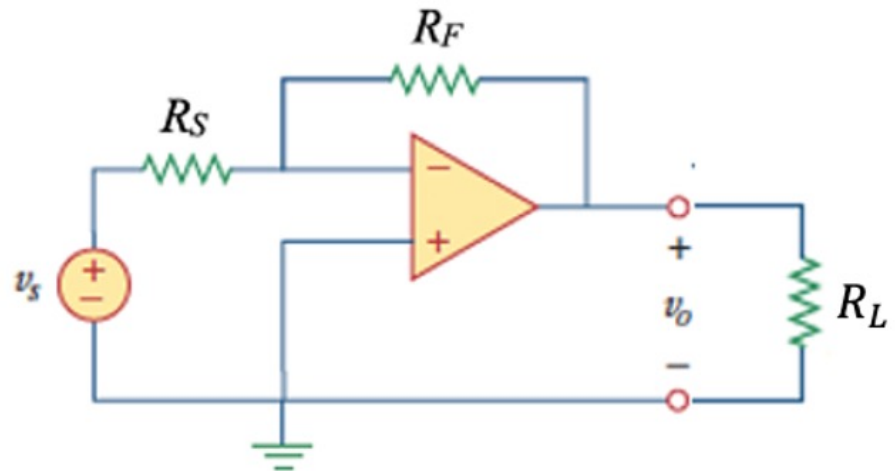- Usually configured with “negative feedback”



Non-Ideal Characteristics

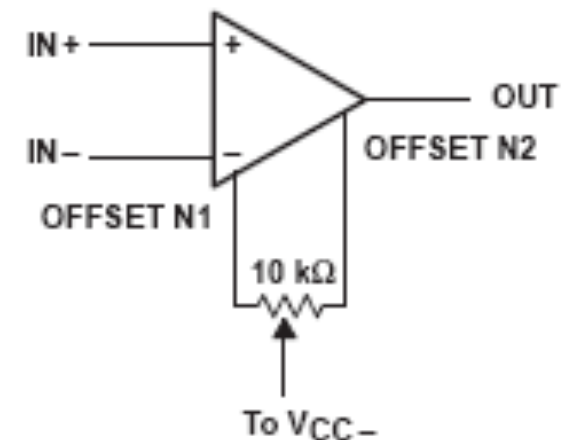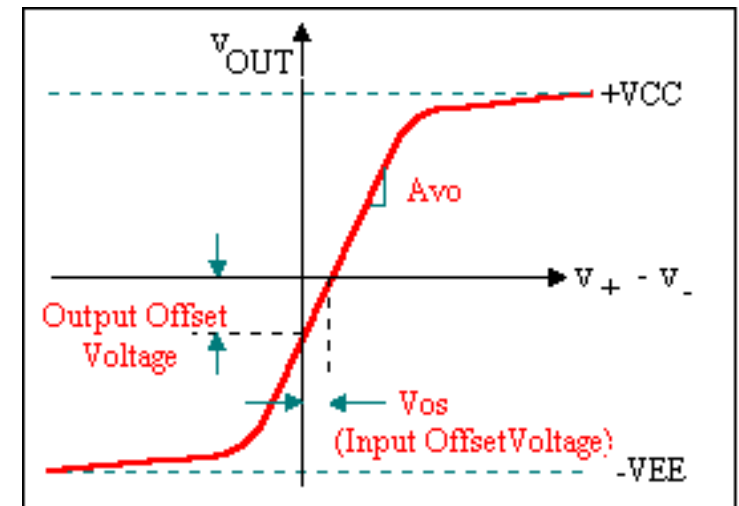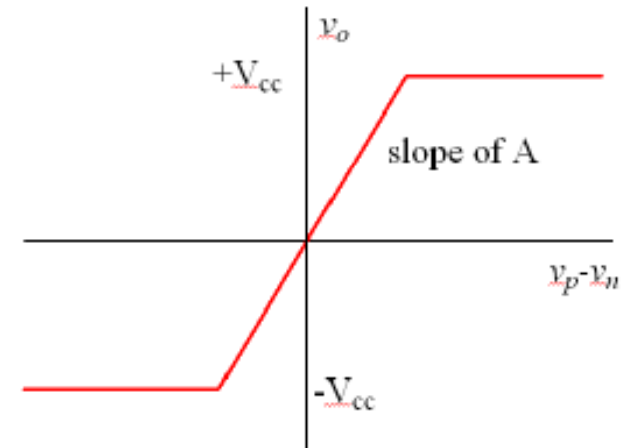- Issue 1 – DC offset voltage
 - Equal input voltages yield non-zero output
 - Large enough to saturate an open loop circuit
 - External compensation is possible
 - 1 mv typical for 741



electrical characteristics at specified free-air temperature, $V_{CC\pm} = \pm 15\text{ V}$, $T_A = 25^\circ\text{C}$ (unless otherwise noted)

| PARAMETER | TEST CONDITIONS | μA741Y | | | UNIT |
|--|---|-------------------|----------|----------|-----------------|
| | | MIN | TYP | MAX | |
| V_{IO} Input offset voltage | $V_O = 0$ | | 1 | 6 | mV |
| $\Delta V_{IO}(\text{adj})$ Offset voltage adjust range | $V_O = 0$ | | ± 15 | | mV |
| I_{IO} Input offset current | $V_O = 0$ | | 20 | 200 | nA |
| I_{IB} Input bias current | $V_O = 0$ | | 80 | 500 | nA |
| V_{ICR} Common-mode input voltage range | | ± 12 | ± 13 | | V |
| V_{OM} Maximum peak output voltage swing | $R_L = 10\text{ k}\Omega$ | ± 12 | ± 14 | | V |
| | $R_L = 2\text{ k}\Omega$ | ± 10 | ± 13 | | |
| A_{VD} Large-signal differential voltage amplification | $R_L \geq 2\text{ k}\Omega$ | 20 | 200 | | V/mV |
| r_i Input resistance | | 0.3 | 2 | | M Ω |
| r_o Output resistance | $V_O = 0$, See Note 5 | | 75 | | Ω |
| C_i Input capacitance | | | 1.4 | | pF |
| CMRR Common-mode rejection ratio | $V_{IC} = V_{ICR\text{min}}$ | 70 | 90 | | dB |
| k_{SVS} Supply voltage sensitivity ($\Delta V_{IO}/\Delta V_{CC}$) | $V_{CC} = \pm 9\text{ V to } \pm 15\text{ V}$ | | 30 | 150 | $\mu\text{V/V}$ |
| I_{OS} Short-circuit output current | | | ± 25 | ± 40 | mA |
| I_{CC} Supply current | $V_O = 0$, No load | | 1.7 | 2.8 | mA |
| P_D Total power dissipation | $V_O = 0$, No load | | 50 | 85 | mW |


† All characteristics are measured under open-loop conditions with zero common-mode voltage unless otherwise specified.


NOTE 5: This typical value applies only at frequencies above a few hundred hertz because of the effects of drift and thermal feedback.

operating characteristics, $V_{CC\pm} = \pm 15\text{ V}$, $T_A = 25^\circ\text{C}$

| PARAMETER | TEST CONDITIONS | μA741Y | | | UNIT |
|----------------------------|---|-------------------|-----|-----|------------------|
| | | MIN | TYP | MAX | |
| t_r Rise time | $V_I = 20\text{ mV}$, $R_L = 2\text{ k}\Omega$ | | 0.3 | | μs |
| Overshoot factor | $C_L = 100\text{ pF}$, See Figure 1 | | 5% | | |
| SR Slew rate at unity gain | $V_I = 10\text{ V}$, $R_L = 2\text{ k}\Omega$, $C_L = 100\text{ pF}$, See Figure 1 | | 0.5 | | V/ μs |

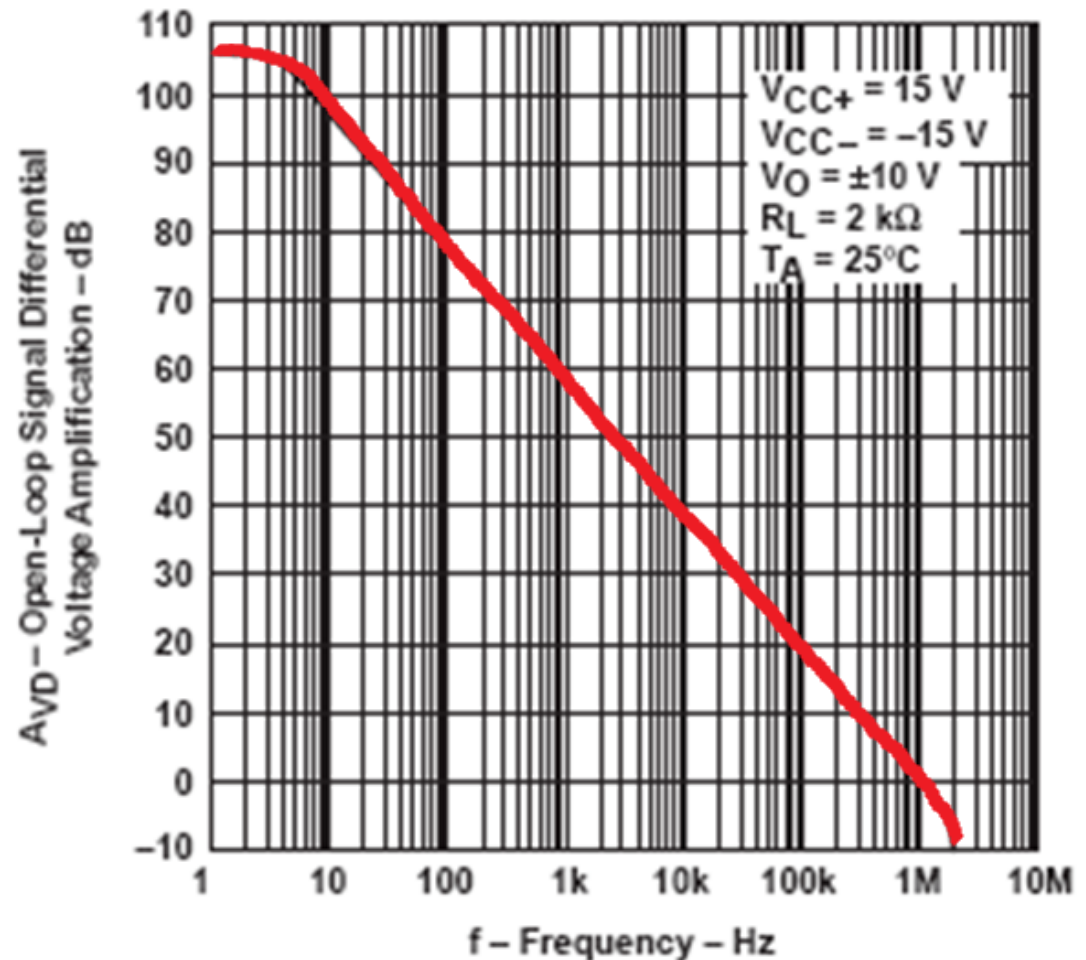- Issue 2 – Open loop gain, A , is finite
 - Decreases with frequency
 - 200,000 typical for a 741 op amp
 - Limits amplifier gain



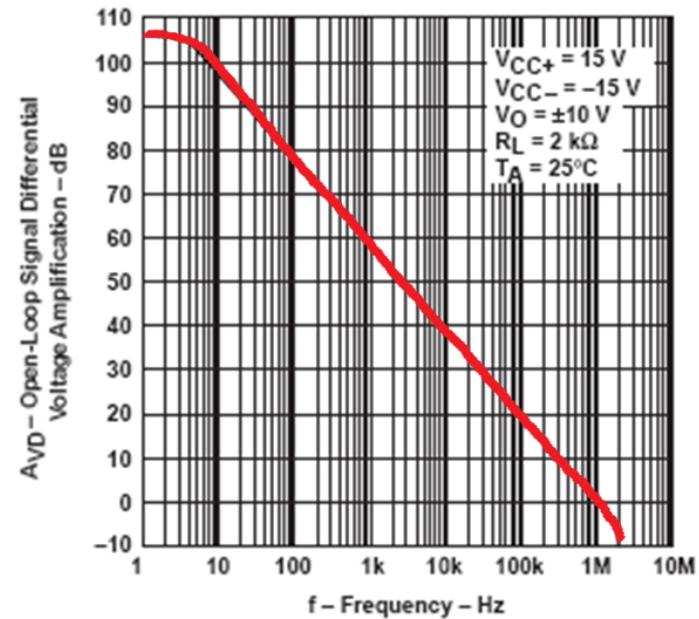

- Notes on this plot:
 - Logarithmic scale for frequency
 - Factor of 10 called a “decade”
 - Gain A is plotted on the vertical scale using units of decibels



$$20 \log_{10} A = 20 \log_{10} 200,000 = 106 \text{ dB}$$

- Note: decibel scale



| mag | dB | mag | dB |
|-----|----|------|-----|
| 1 | 0 | | |
| 2 | 3 | 0.5 | -3 |
| 10 | 20 | 0.1 | -20 |
| 100 | 40 | 0.01 | -40 |

For audio sound levels, whisper to normal conversation to a motorcycle are 30 dB jumps each

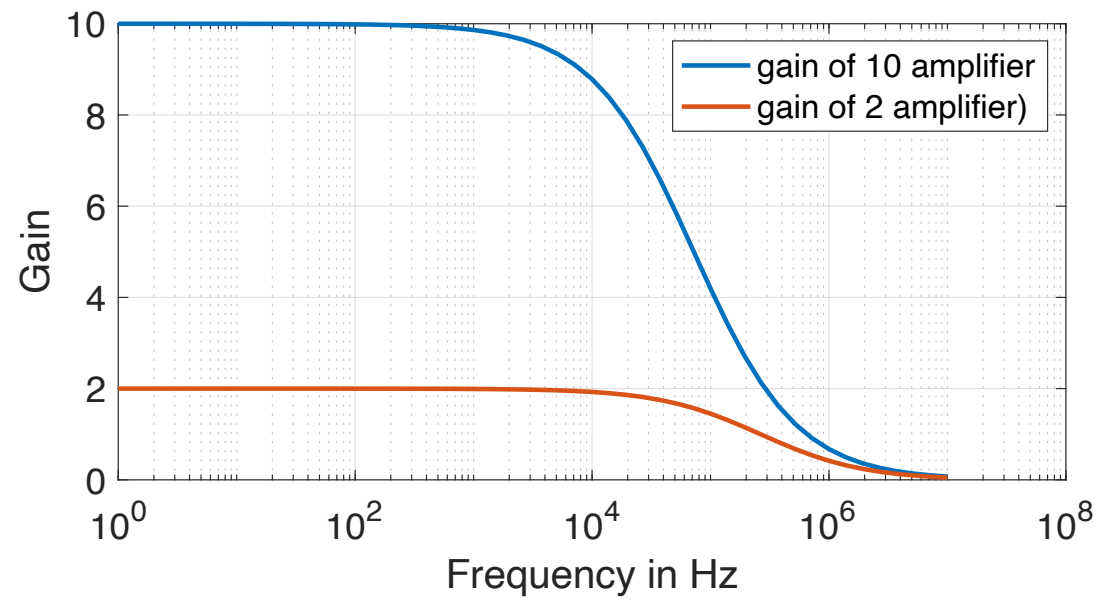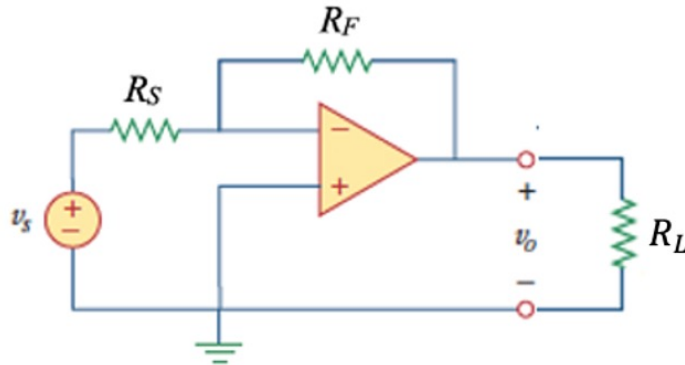- Impact of decreasing A on the gain of an inverting amplifier:



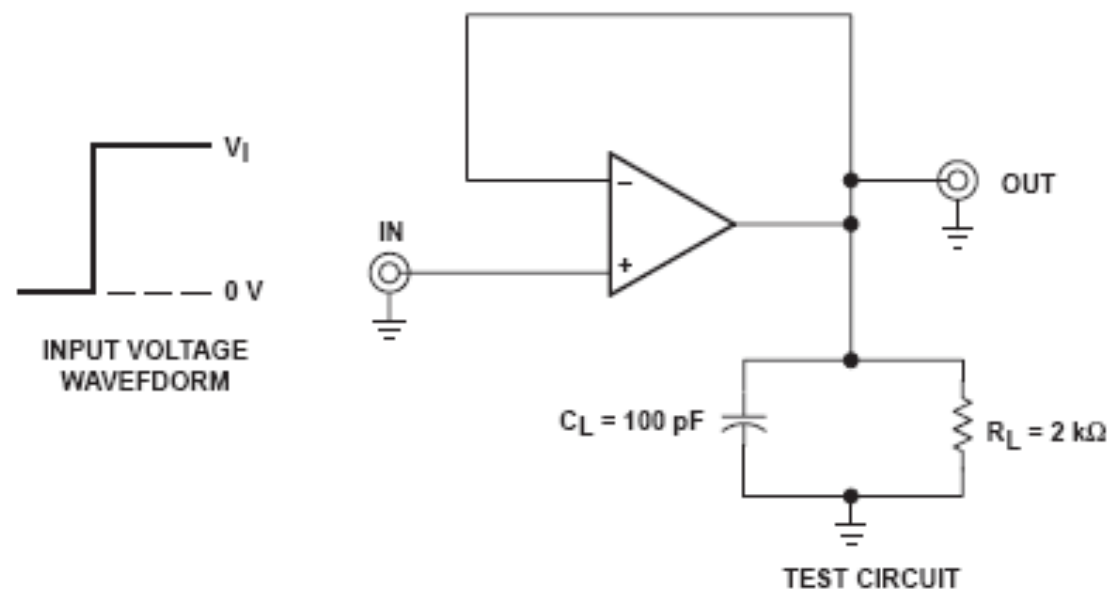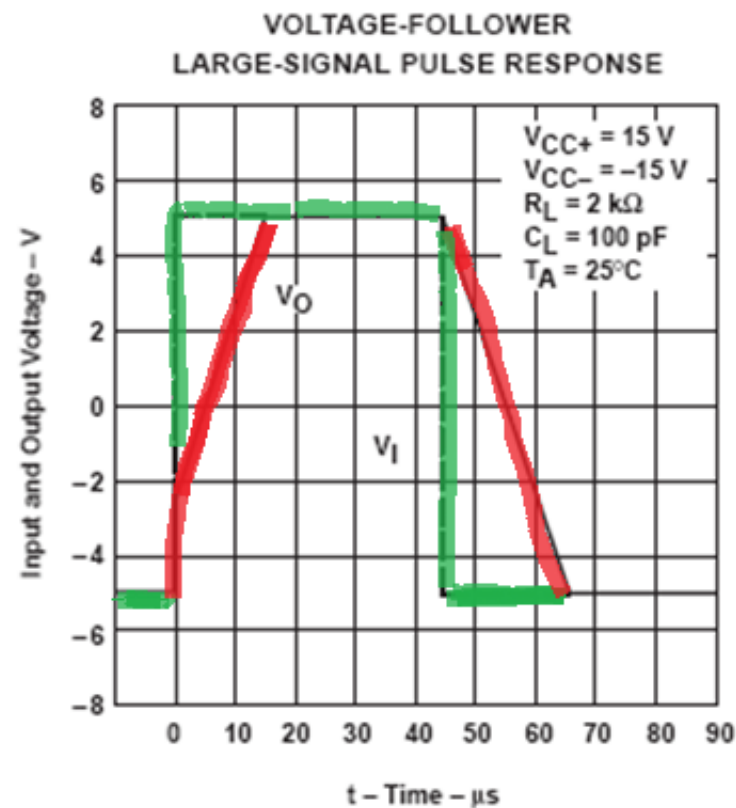- Issue 3 – slow response to voltage jumps: “slew rate”
 - Essentially the slope of the response
 - Measured in $V/\mu s$, 0.5 typical for 741



electrical characteristics at specified free-air temperature, $V_{CC\pm} = \pm 15\text{ V}$, $T_A = 25^\circ\text{C}$ (unless otherwise noted)

| PARAMETER | | TEST CONDITIONS | μA741Y | | | UNIT |
|-----------------------------|--|---|-------------------|----------|----------|-----------------|
| | | | MIN | TYP | MAX | |
| V_{IO} | Input offset voltage | $V_O = 0$ | | 1 | 6 | mV |
| $\Delta V_{IO(\text{adj})}$ | Offset voltage adjust range | $V_O = 0$ | | ± 15 | | mV |
| I_{IO} | Input offset current | $V_O = 0$ | | 20 | 200 | nA |
| I_{IB} | Input bias current | $V_O = 0$ | | 80 | 500 | nA |
| V_{ICR} | Common-mode input voltage range | | ± 12 | ± 13 | | V |
| V_{OM} | Maximum peak output voltage swing | $R_L = 10\text{ k}\Omega$ | ± 12 | ± 14 | | V |
| | | $R_L = 2\text{ k}\Omega$ | ± 10 | ± 13 | | |
| A_{VD} | Large-signal differential voltage amplification | $R_L \geq 2\text{ k}\Omega$ | 20 | 200 | | V/mV |
| r_i | Input resistance | | 0.3 | 2 | | M Ω |
| r_o | Output resistance | $V_O = 0$, See Note 5 | | 75 | | Ω |
| C_i | Input capacitance | | | 1.4 | | pF |
| CMRR | Common-mode rejection ratio | $V_{IC} = V_{ICR\text{min}}$ | 70 | 90 | | dB |
| k_{SVS} | Supply voltage sensitivity ($\Delta V_{IO}/\Delta V_{CC}$) | $V_{CC} = \pm 9\text{ V to } \pm 15\text{ V}$ | | 30 | 150 | $\mu\text{V/V}$ |
| I_{OS} | Short-circuit output current | | | ± 25 | ± 40 | mA |
| I_{CC} | Supply current | $V_O = 0$, No load | | 1.7 | 2.8 | mA |
| P_D | Total power dissipation | $V_O = 0$, No load | | 50 | 85 | mW |

† All characteristics are measured under open-loop conditions with zero common-mode voltage unless otherwise specified.

NOTE 5: This typical value applies only at frequencies above a few hundred hertz because of the effects of drift and thermal feedback.


operating characteristics, $V_{CC\pm} = \pm 15\text{ V}$, $T_A = 25^\circ\text{C}$

| PARAMETER | | TEST CONDITIONS | μA741Y | | | UNIT |
|-----------|-------------------------|---|-------------------|-----|-----|------------------|
| | | | MIN | TYP | MAX | |
| t_r | Rise time | $V_I = 20\text{ mV}$, $R_L = 2\text{ k}\Omega$ | | 0.3 | | μs |
| | Overshoot factor | $C_L = 100\text{ pF}$, See Figure 1 | | 5% | | |
| SR | Slew rate at unity gain | $V_I = 10\text{ V}$, $R_L = 2\text{ k}\Omega$, $C_L = 100\text{ pF}$, See Figure 1 | | 0.5 | | V/ μs |



The Inverting Amplifier

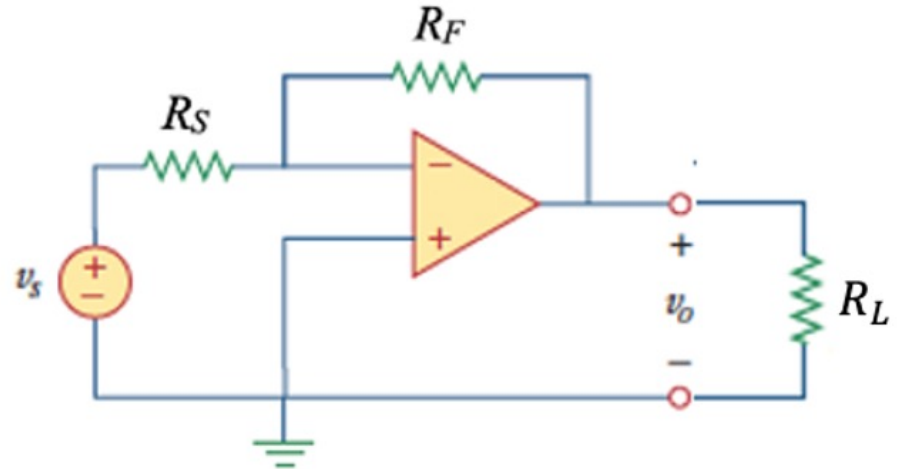- Detailed analysis yields (ELE 212 lecture):




$$\frac{v_o}{v_s} = - \frac{R_i R_L (R_F A - R_o)}{R_L (R_S + R_i) (R_F + R_o) + (A + 1) R_S R_i R_L + R_o (R_S R_i + R_F R_i + R_S R_F)}$$

- Under normal conditions, approximate result

$$\frac{v_o}{v_s} \approx - \frac{R_F}{R_S}$$


Other Op Amp Uses

- Inverting amplifier

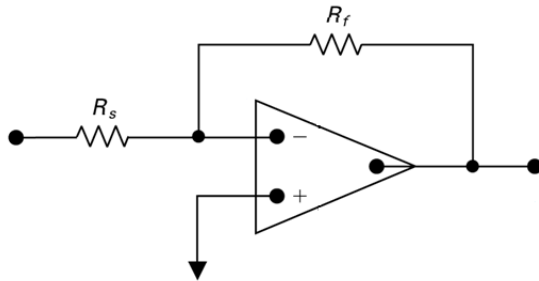


$$v_o = -\frac{R_F}{R_S} v_s$$

- Non-inverting amplifier

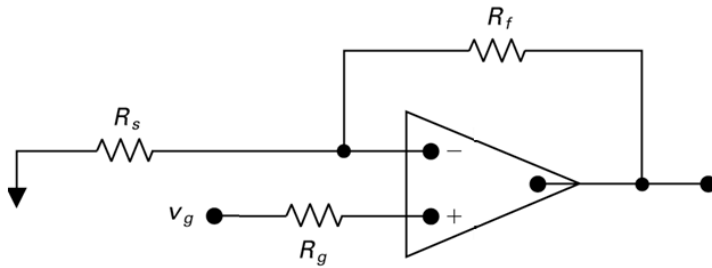


$$v_o = \left(1 + \frac{R_F}{R_1}\right) v_s$$

- Difference amplifier

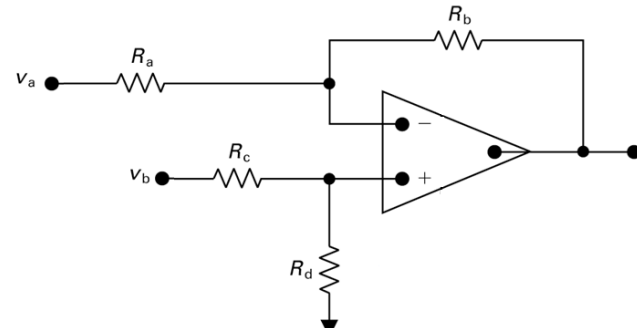

$$v_o = \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1}\right) v_2 - \frac{R_2}{R_1} v_1$$

- Summing amplifier

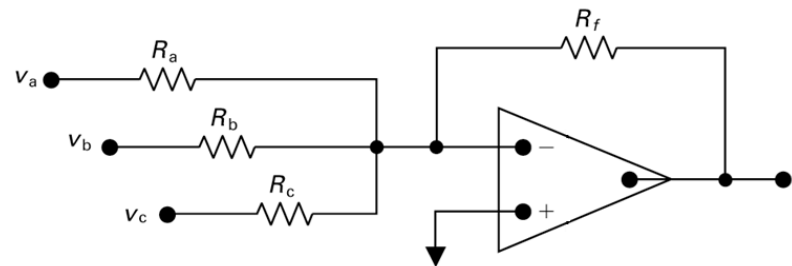

$$v_o = -\left(\frac{R_F}{R_1} v_1 + \frac{R_F}{R_2} v_2 + \frac{R_F}{R_3} v_3\right)$$

Specifics for next week

- Continue work on Exercise 1 (programming) and Exercise 3 (simulation)
- Lab 4 – 75 points (pairs)
 - Instructions and pairings posted on ELE 215 website
 - Summary sheets available in lab rooms and on website
 - Due by 5 PM Wednesday Mar 11