

**ELE 215 Summary Report Form**  
**Exercise 3 – due 9 AM on Mar 23, 2026**

Score: / 55

Name: \_\_\_\_\_ HW ID (just the last 3 digits): \_\_\_\_\_

1. Circuit analysis for prescribed components (same as submitted online; points given there):

– Results:  $v_0 =$  \_\_\_\_\_  $i_0 =$  \_\_\_\_\_

2. Variational Analysis:

– Statistics from 1000 trials:

	mean	$x$ for 90% of the data	% range
$v_0$			
$i_0$		XXXXXX	XXXXXX

3. Reporting:

– Attach the two histograms as a single separate page after this sheet. Label the figures properly.