

ELE 215 Summary Report Form
Lab 2 – due 5 PM on Feb 18, 2026

Score:

/ 60

Name: _____

HW ID (just the last 3 digits): _____

1. Putting in some basic components:

d) TA check of 556 installed properly (before soldering!): _____

2. Getting the clock signals:

b) TA check of clocks: _____

3. Adding the counters:

d) TA check of counters: _____

4. Adding the LEDs:

d) TA check of fully working circuit: _____

Penalty for incorrect IC/LED placement or generally not following instructions:
