

ELE 215 Summary Report Form
Lab 1 – due 5 PM on Feb 4, 2026

Score: /45

Names: _____

HW IDs (just the last 3 digits): _____


1. Build the first circuit:

a) Resistor information; include units, please:

	Nominal resistance	Measured resistance
R_1		
R_2		


c) Initial setup working:

TA check:


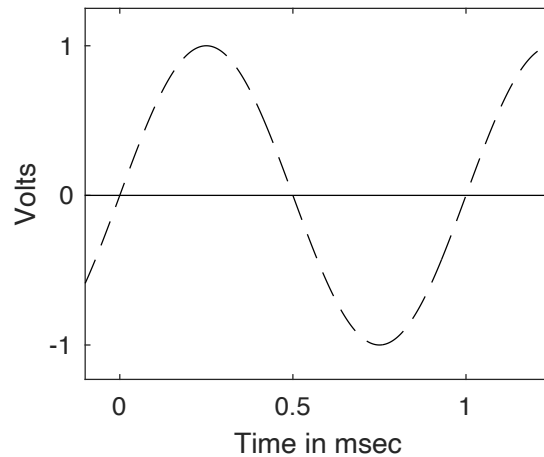


2. Test the linear circuit:

a) Scaled version:

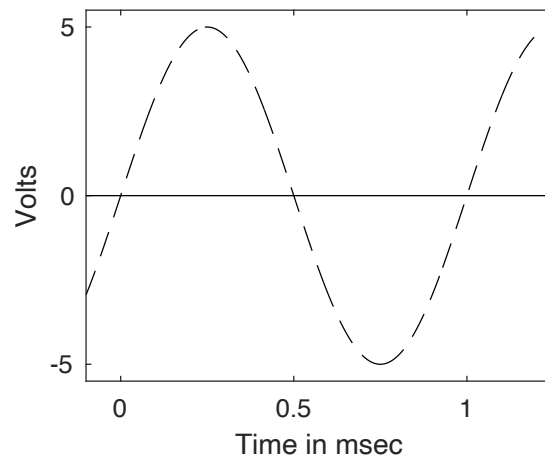

b) Square wave input:

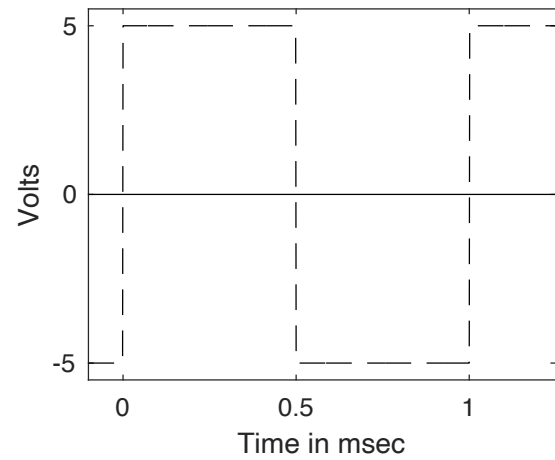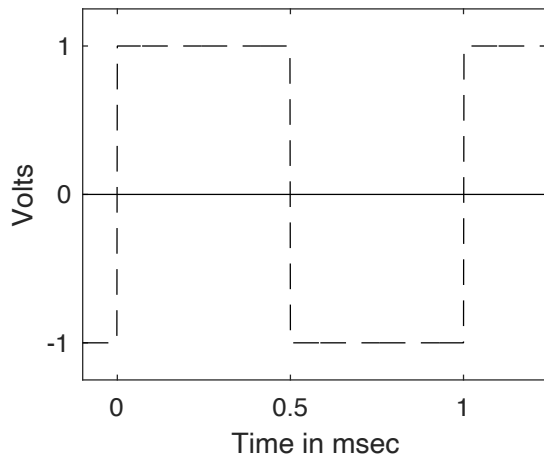

3. Test the nonlinear circuit:

b) Sinusoid:

